

# KS16001 LABORATORY 1 TEST

Using Proteus Software, answer all questions (40 marks).  
Screenshot your simulated circuit and paste in the answer area.  
Convert this paper to the pdf file and submit to SmartV3.

- For the circuit in Figure 1, set the resistance value for R5 to the last two digits of your student number (Example: BK19111234, so R5 will be **34KILO** ohm).


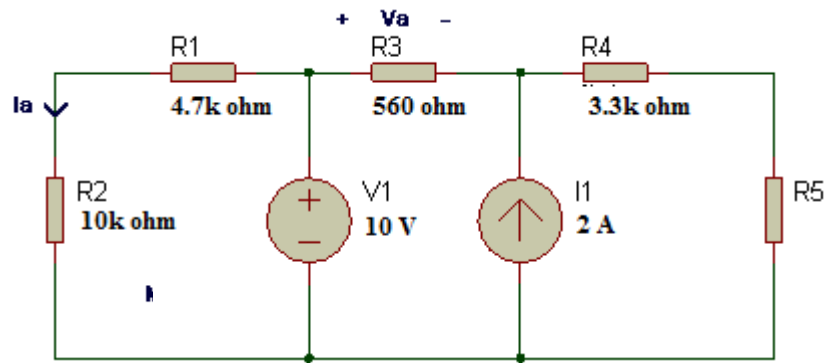



Figure 1

- Find **Va** and **Ia**.

Answer: (Paste your simulated circuit)

(4 marks)

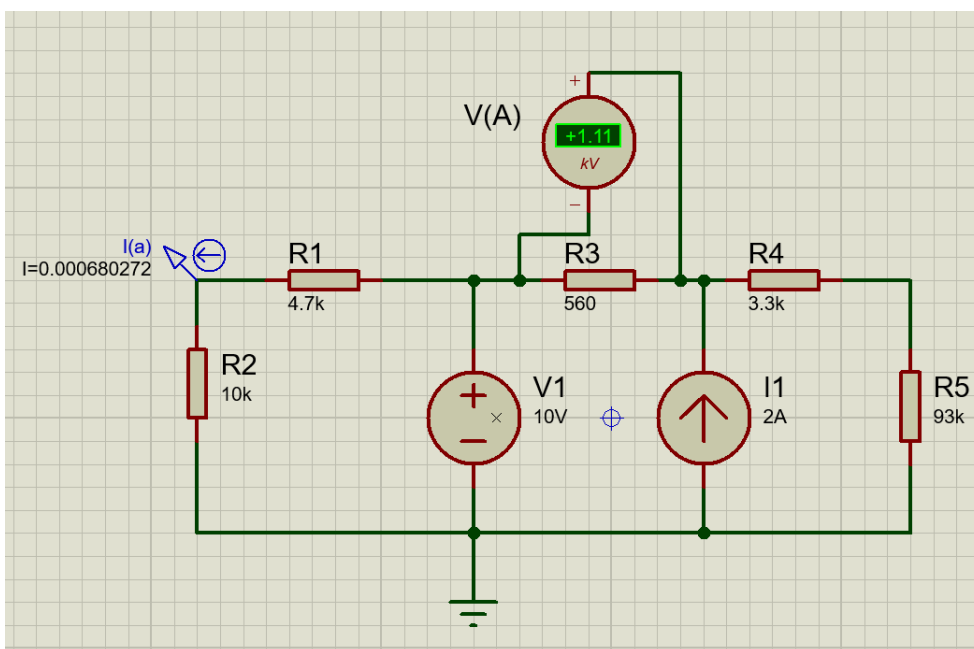

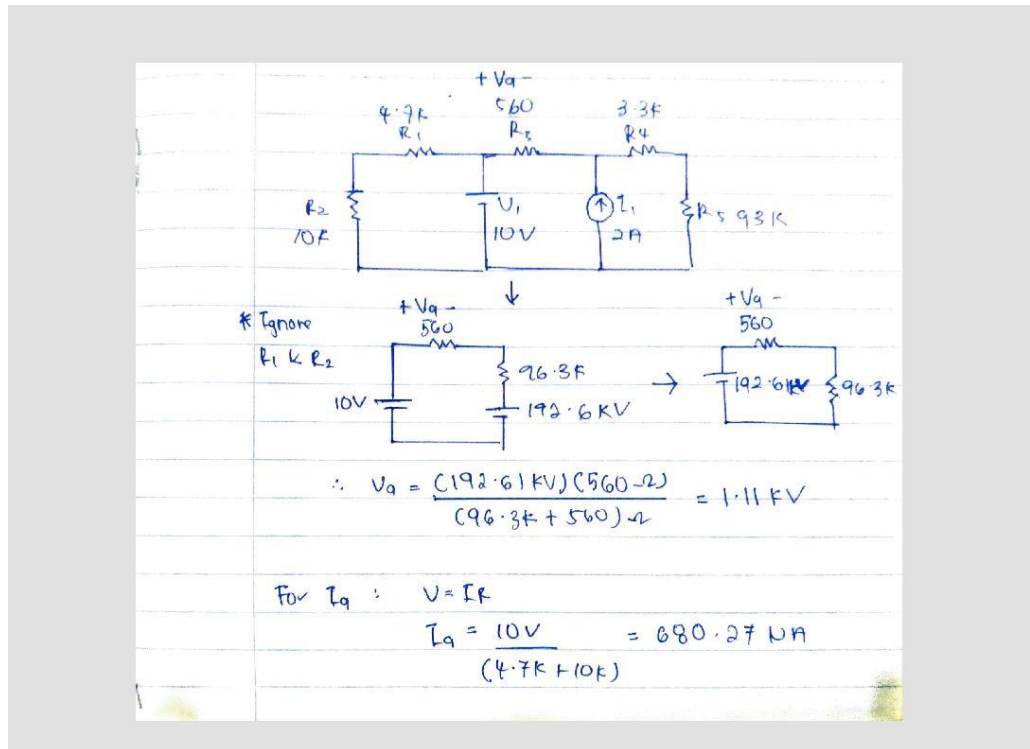



Hence  $V_a = 1.11 \text{ kV}$ ,  $I_a = 680.27 \mu\text{A}$

b. Determine the power dissipated in the resistor  $R_4$ .

Answer: (Paste your simulated circuit)

(6 marks)

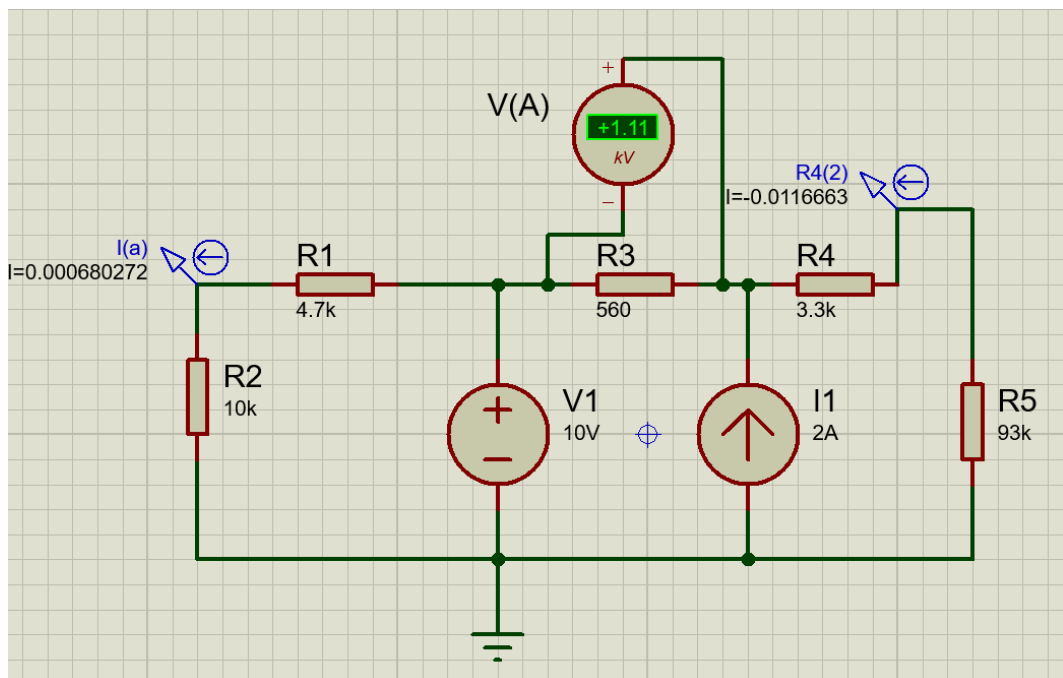

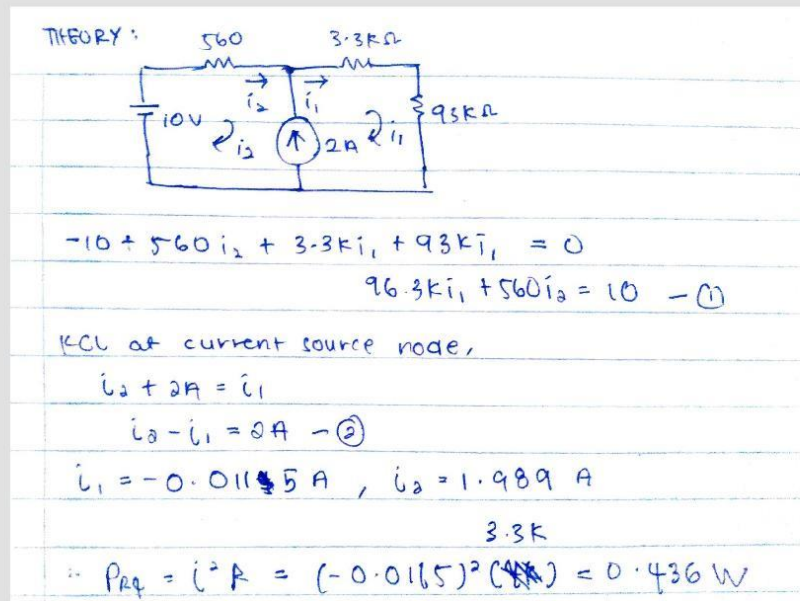

Hence, Measured Power Dissipated by R4,


$$P_{R4} = I^2 R = (-0.0116663)^2 (3.3k) = 0.449W$$



c. Obtain its Thevenin Equivalent circuit 'seen' by R5 (assume R5 is the Load Resistor).

Answer: (Paste the circuit to find  $R_{TH}$ ,  $V_{TH}$  and the Thevenin circuit).

(10 marks)

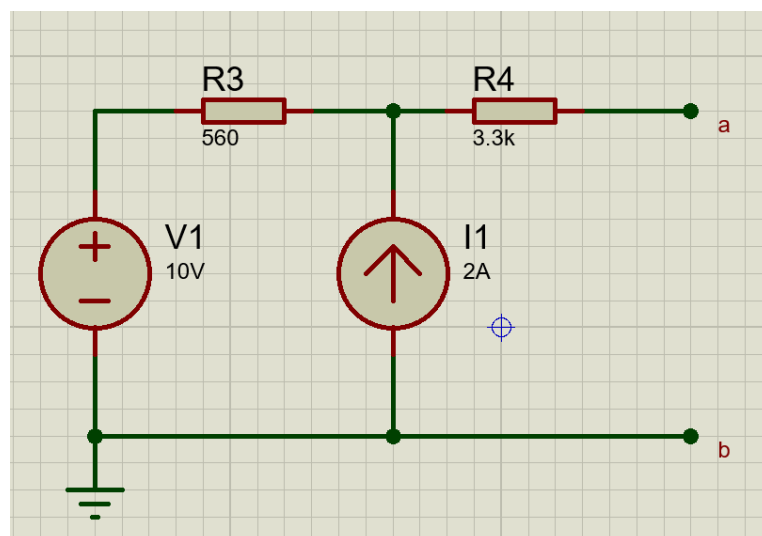
- We make an observation that R1 and R2 will have no influence on the behavior of the circuit with respect to terminal a, b. This is because they are in parallel with an ideal voltage source.
- Given that R5 is Load Resistor, hence, the circuit can be simplified:



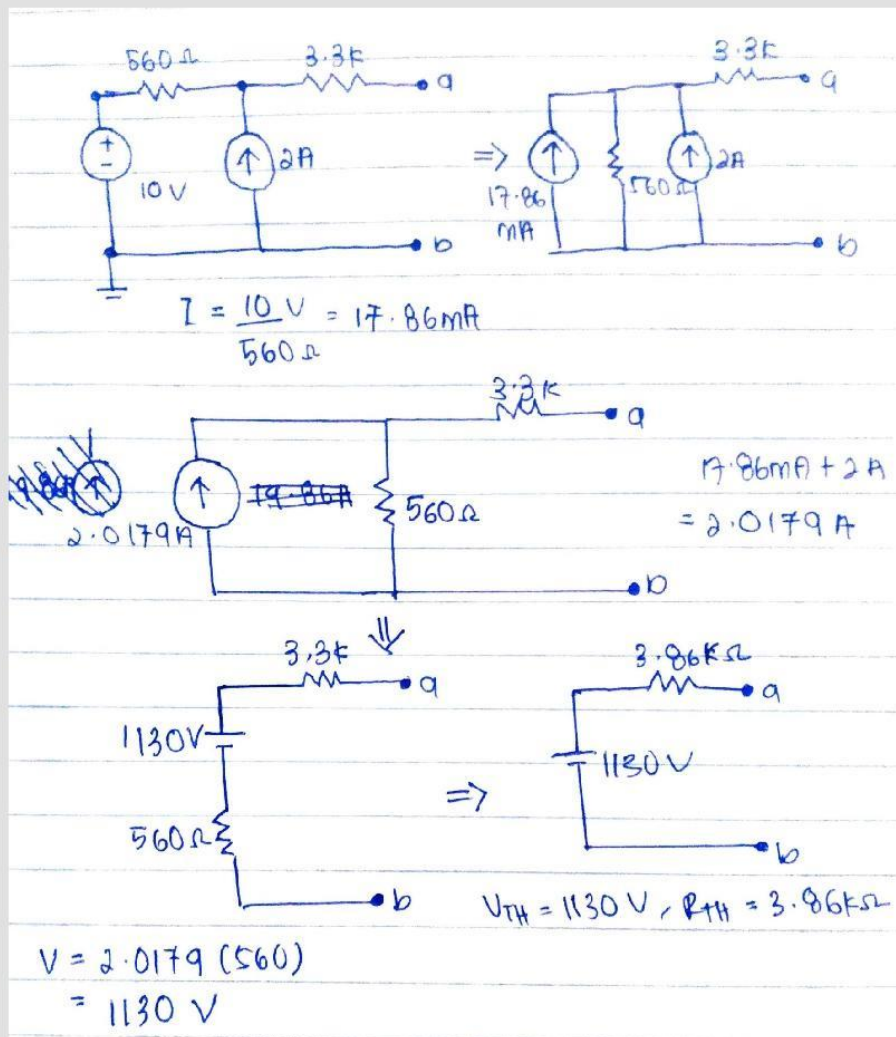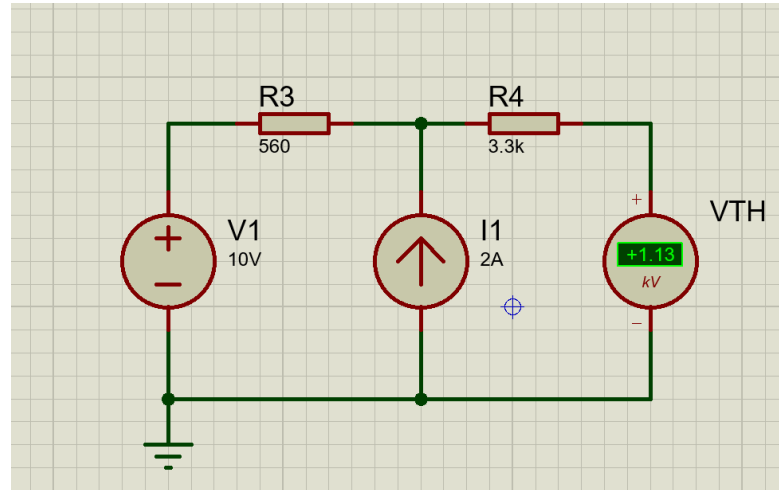

Hence,  $R_{TH} = 3.86k\Omega$  ,  $V_{TH} = 1.13kV$

And Thevenin Circuit:

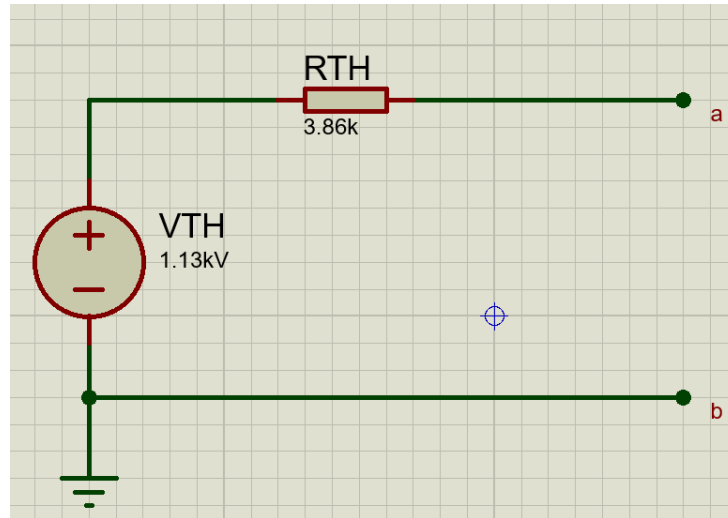

2. Construct the circuit in Figure 2. Set  $V_{in}$  to 5000 Hz square wave of  $m$  Volts peak-to-peak amplitude,  $R = 1\text{k}\Omega$  and  $C = 0.05\mu\text{F}$  ( $m$  is the last digit of your student number, if the last digit is 0, take the 2<sup>nd</sup> last digit and so on).


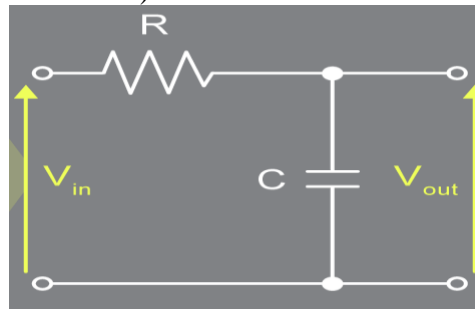


Figure 2

- a. Simulate, screenshot and paste the  $V_{in}$  and  $V_{out}$  signals.

Answer:


(2 marks)

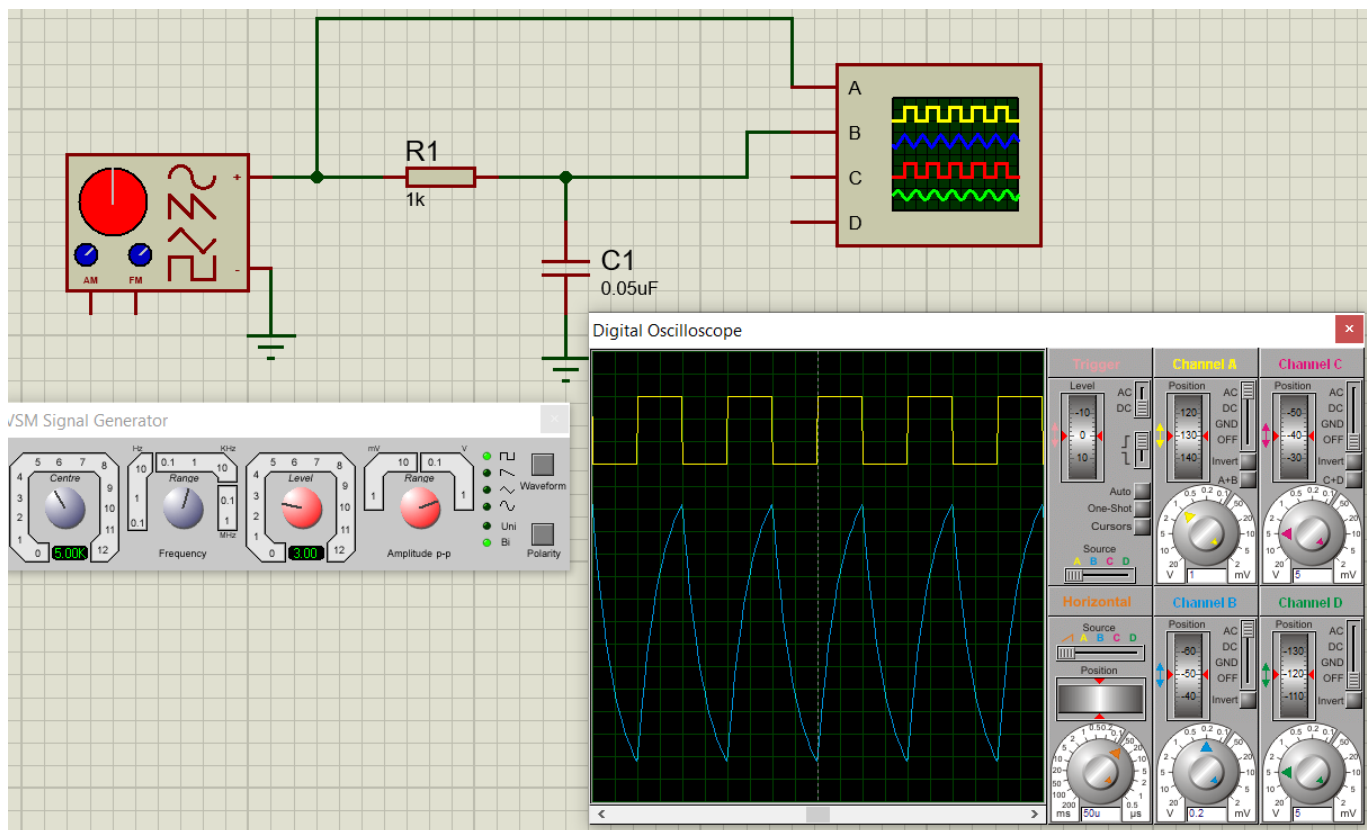

- b. Measure the peak to peak of the  $V_{out}$  signal and phase shift.


Answer:

(6 marks)

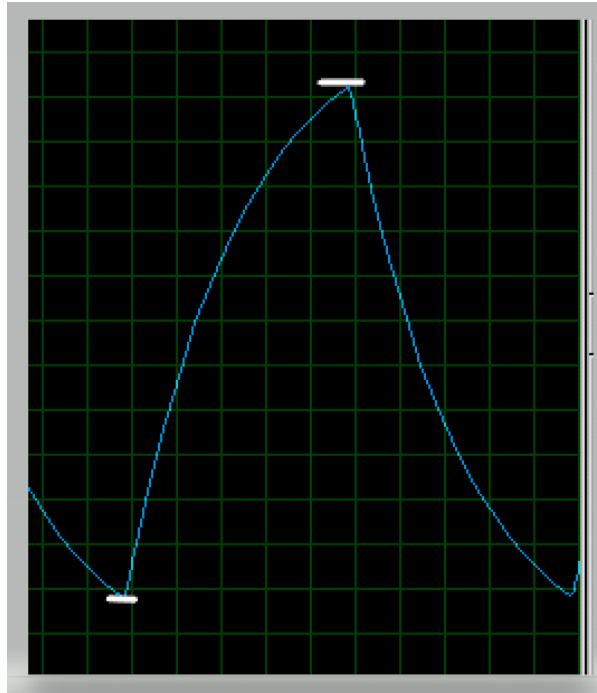

$$V_{out_{p-p}} = 11 \times 0.2 = 2.2V$$

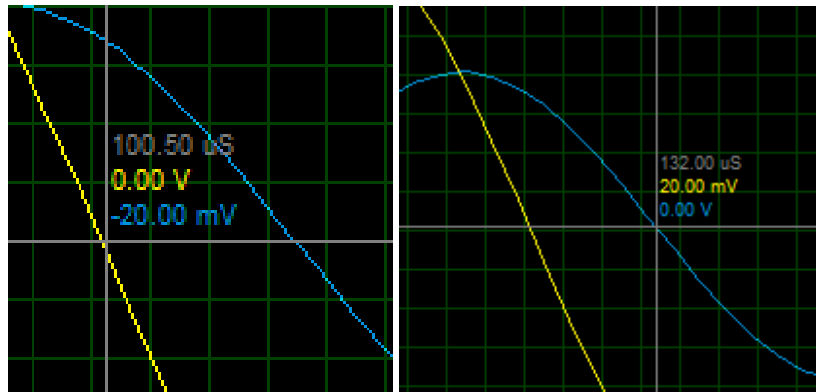For phase shift, change the square wave to sine wave graph to calculate  $\Delta t$ ,



$$\theta = f \times \Delta t \times 360 = 5000Hz \times (133.00\mu s - 100.50\mu s) \times 360^\circ = 58.5^\circ$$

3. Connect and simulate the circuit in Figure 3.  $V_{in}$  is 1000 Hz, 1V<sub>pp</sub>,  $V_{DD}$  is 10 V and  $V_{SS}$  is -10V. Set R3 to the last two digits of your student number in KILO ohm as in Question 1.


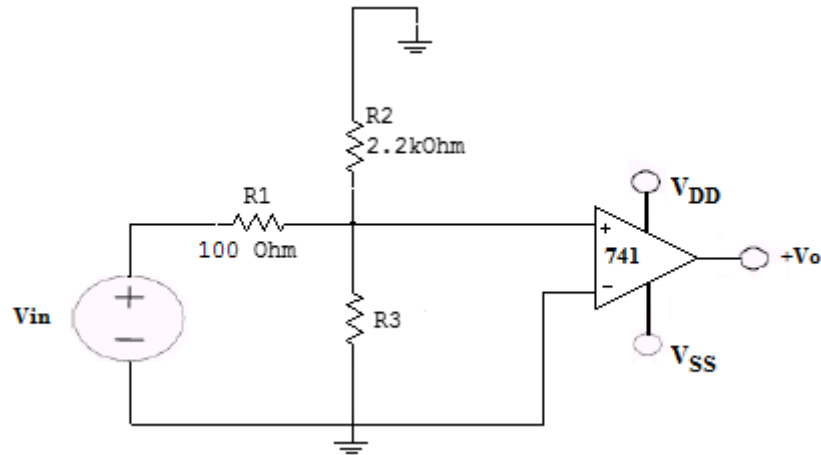


Figure 3


- a. Screenshot and paste the  $V_{in}$  and  $V_o$  signals.

Answer:

(4 marks)

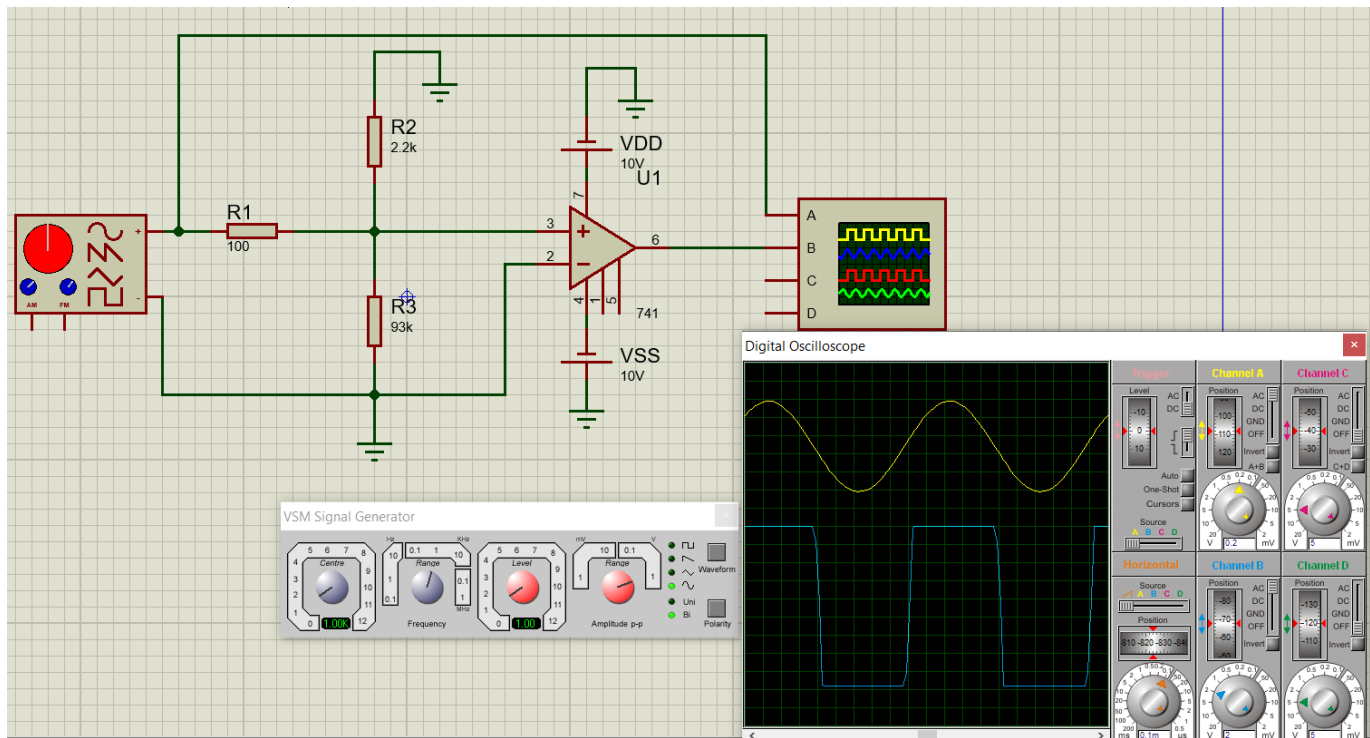



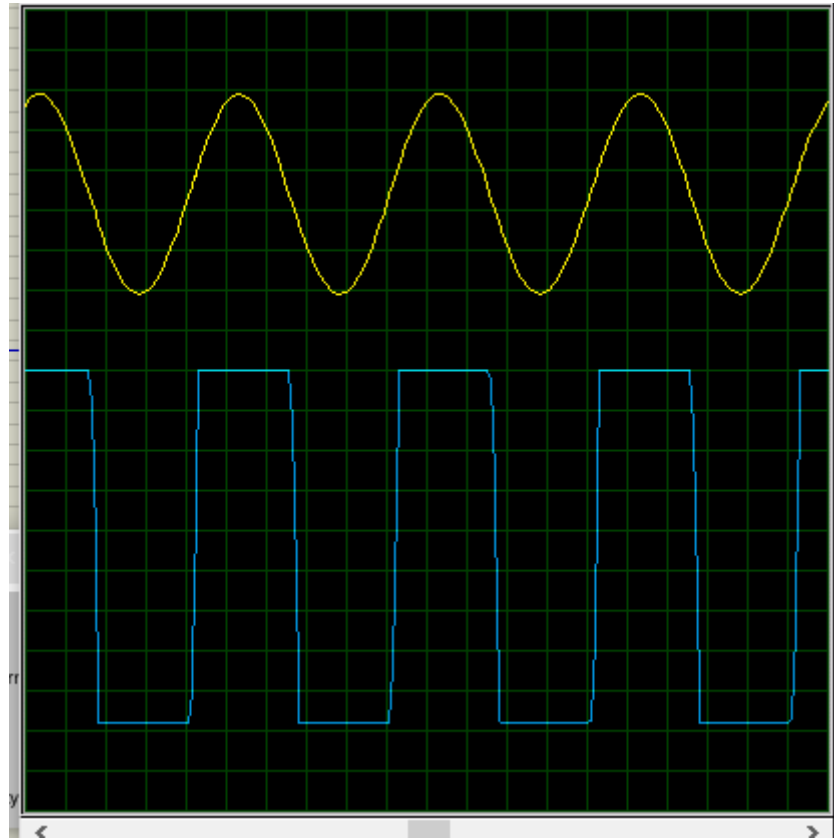


- b. By maintaining the R3 value, modify the circuit to get gain of 2. Screenshot and paste your circuit, Vin and Vo signals.


Answer:

(6 marks)

**Method 1:**

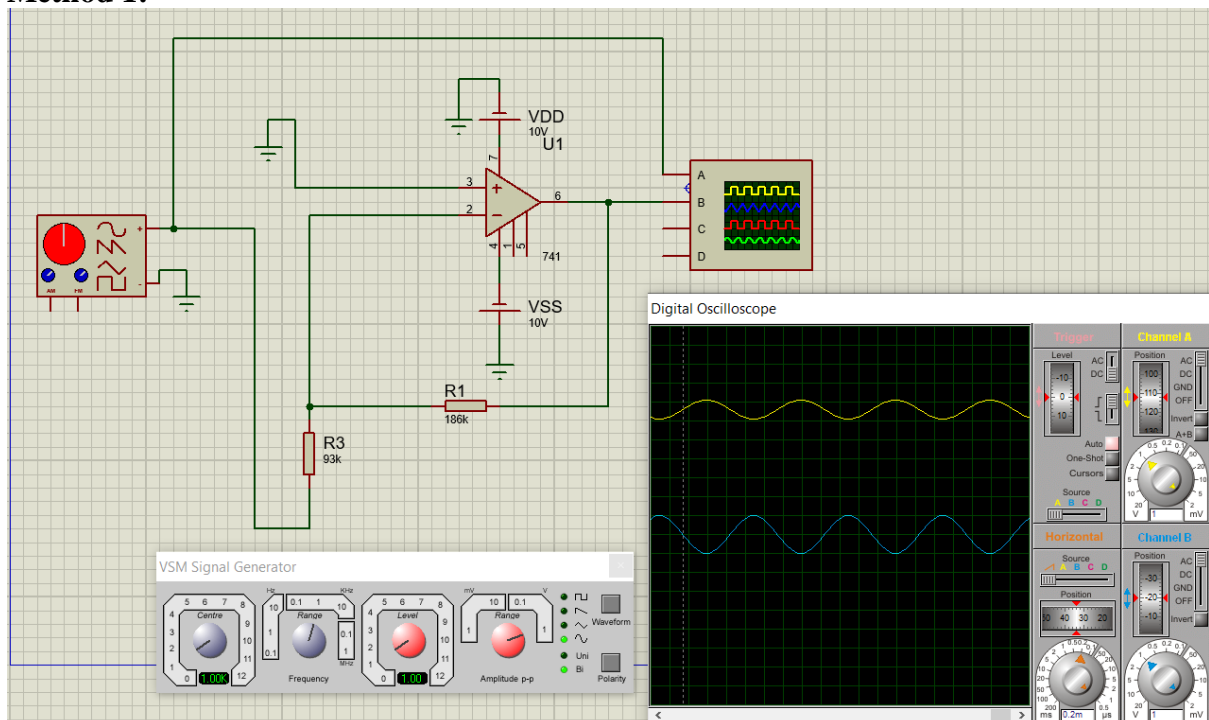

### Digital Oscilloscope

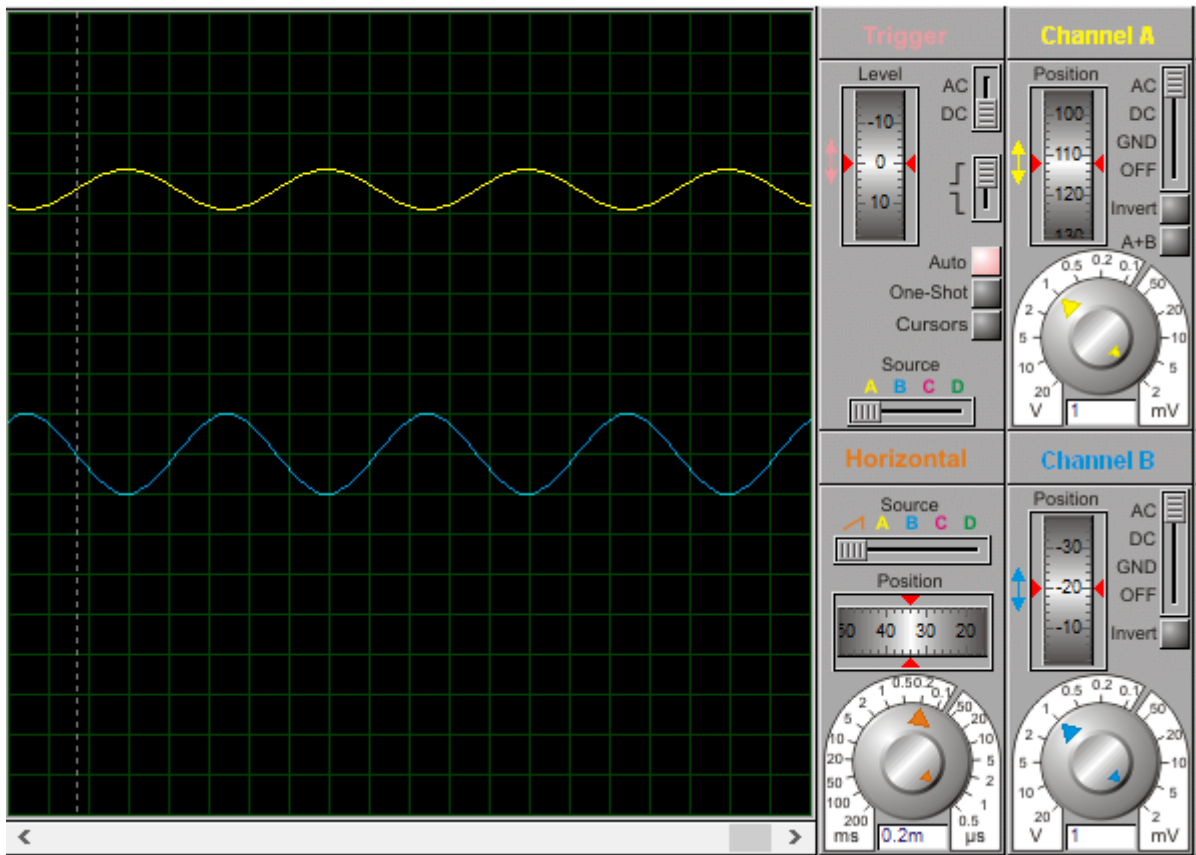

Hence,



Theory Gain:

$$-\frac{R1}{R3} = -\frac{186k}{93k} = -2 \text{ (where (-) sign indicates } 180^\circ \text{ phase shift)}$$

Measured Gain:

$$\frac{V_{out}}{V_{in}} = \frac{2V}{1V} = 2$$

# KS16001 LABORATORY 1 TEST

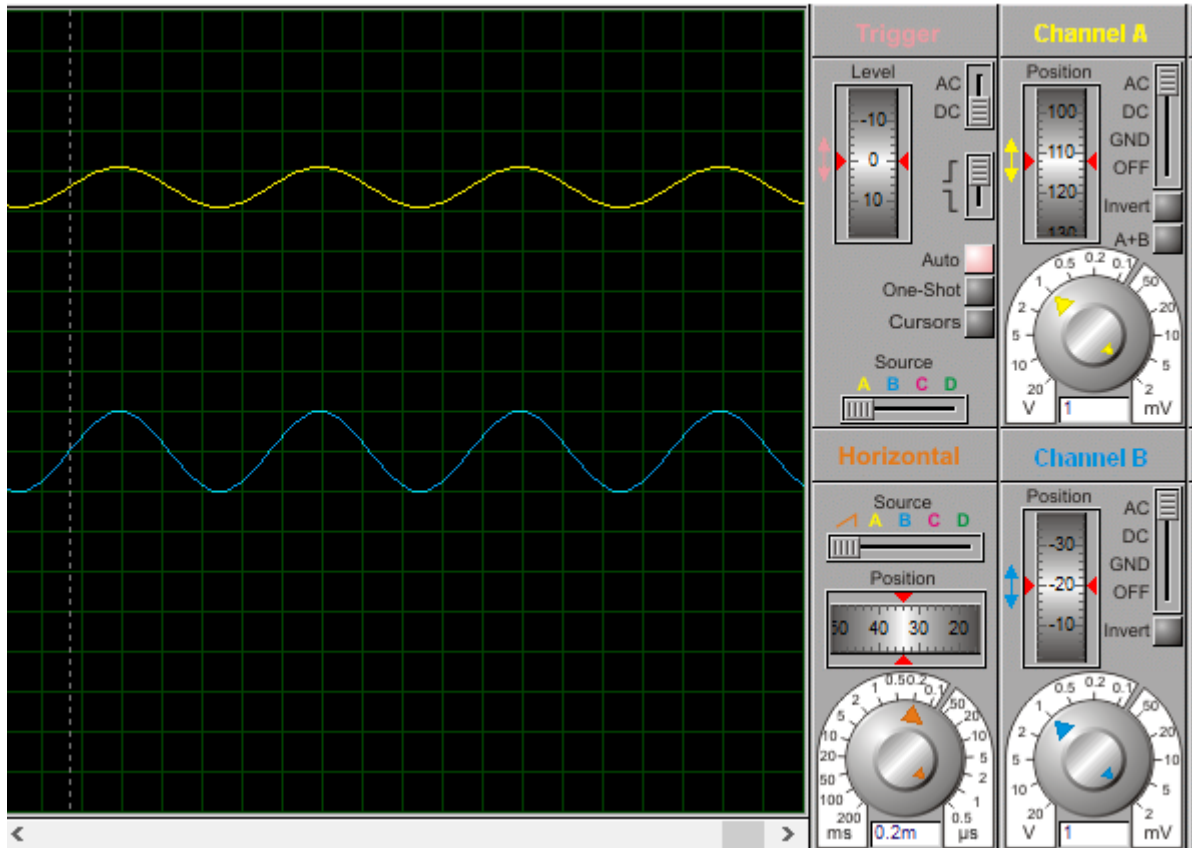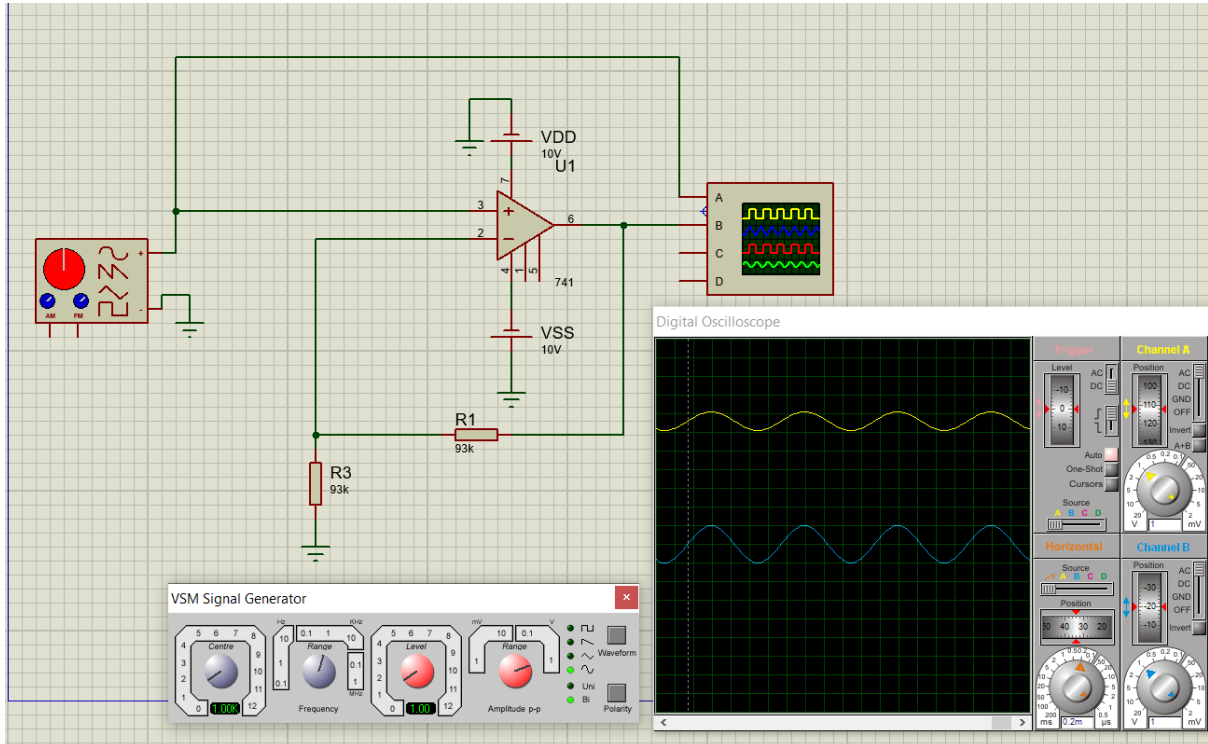



Theory Gain:

$$1 + \frac{R1}{R3} = 1 + \frac{93k}{93k} = 2$$

Measured Gain:

$$\frac{V_{out}}{V_{in}} = \frac{2V}{1V} = 2$$

## Method 3:

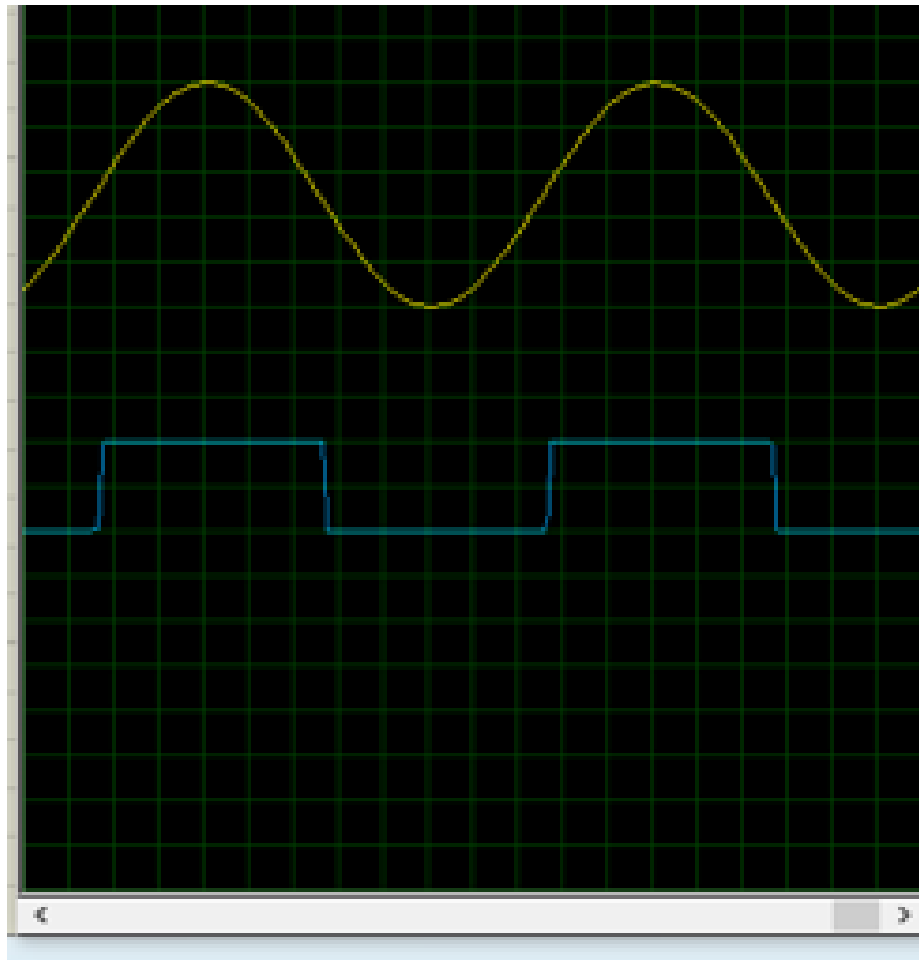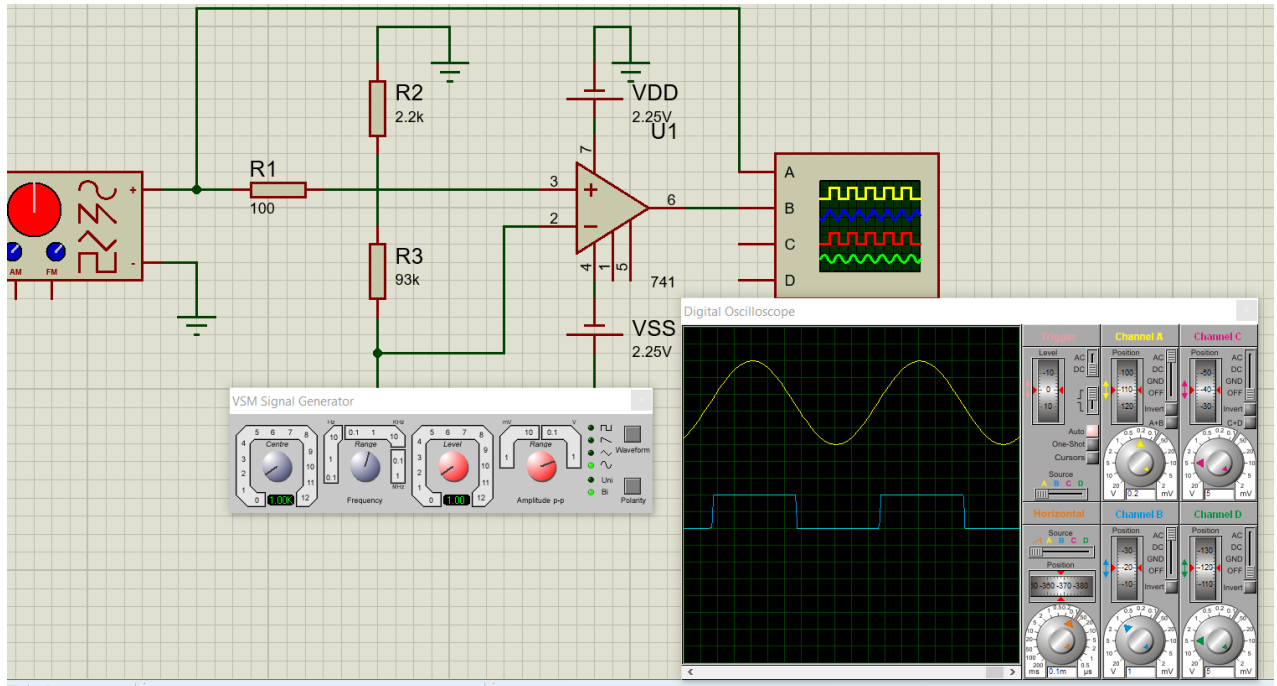

- I tried to modify the value of  $VDD = 2.25V$  and  $VSS = -2.25V$  while the other still have the same value, hence,

$$\text{Gain} = \frac{V_o}{V_i} = \frac{2V}{1V} = 2$$


- c. For the modified circuit in b. What is the maximum amplitude of  $V_{in}$  before the  $V_o$  starts to distort? Screenshot and paste your simulated circuit.

Answer:


(2 marks)

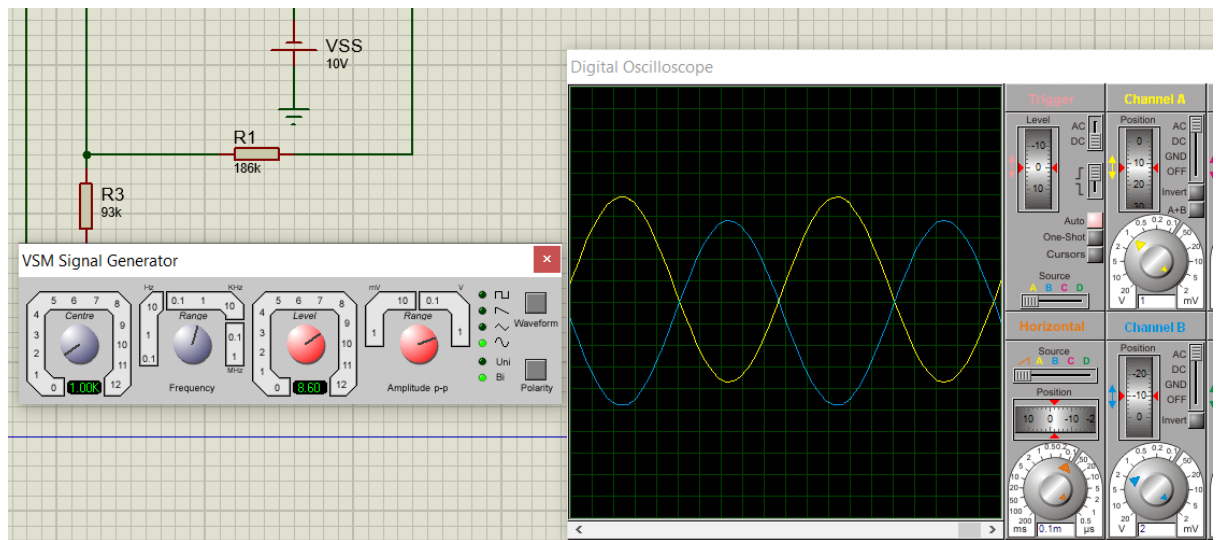**Method 1:**

- Before Distort, amplitude =  $\frac{8.60}{2} = 4.30$



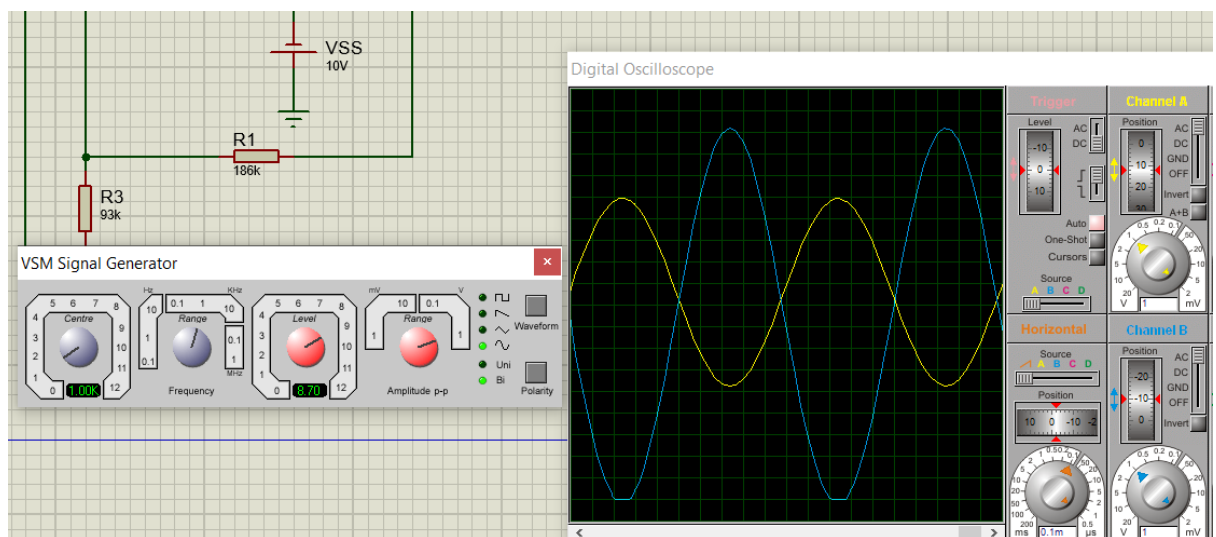
- Start Distort, clipping happened at the bottom part of  $V_{out}$ , amplitude =  $\frac{8.70}{2} = 4.35$




Hence, the maximum amplitude of  $V_{in}$  before the  $V_o$  starts to distort is  $A = 4.30$ .

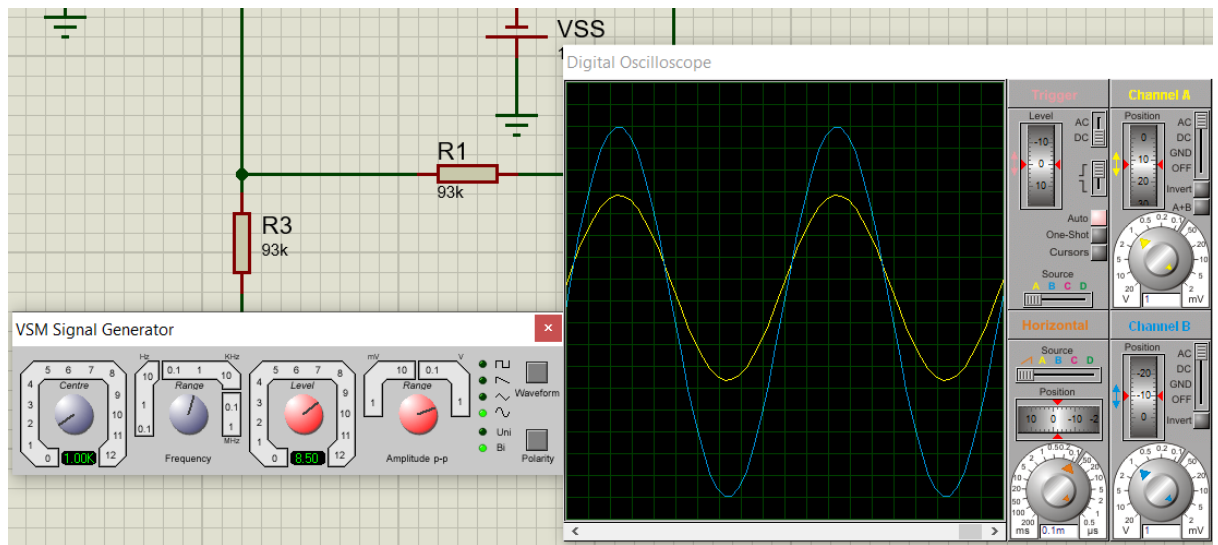**Method 2:**

- Before Distort, amplitude =  $\frac{8.50}{2} = 4.25$



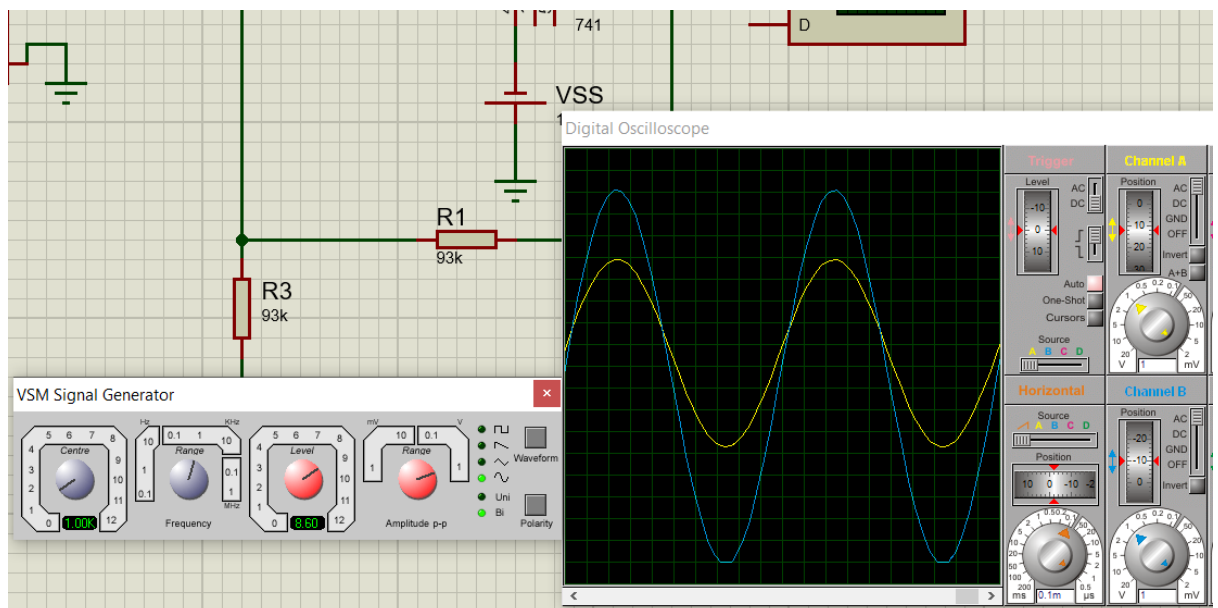
- Start Distort, clipping happened at the bottom part of Vout, amplitude =  $\frac{8.60}{2} = 4.30$




Hence, the maximum amplitude of  $V_{in}$  before the  $V_o$  starts to distort is  $A = 4.25$ .
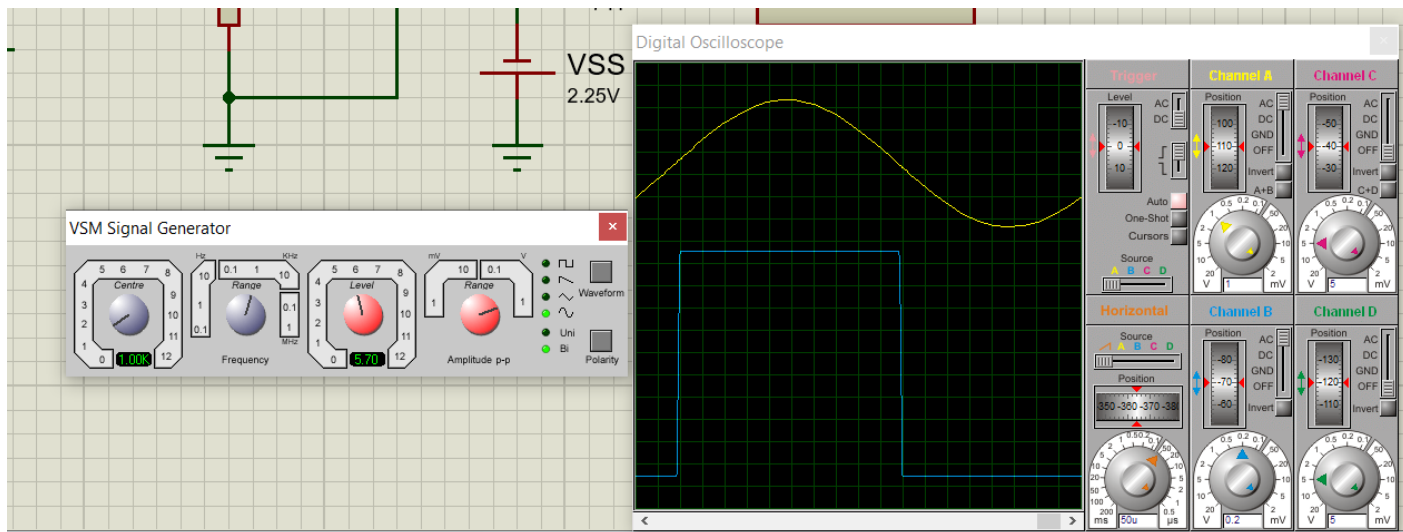
## Method 3:

- Before Distort, amplitude =  $\frac{5.70}{2} = 2.85$



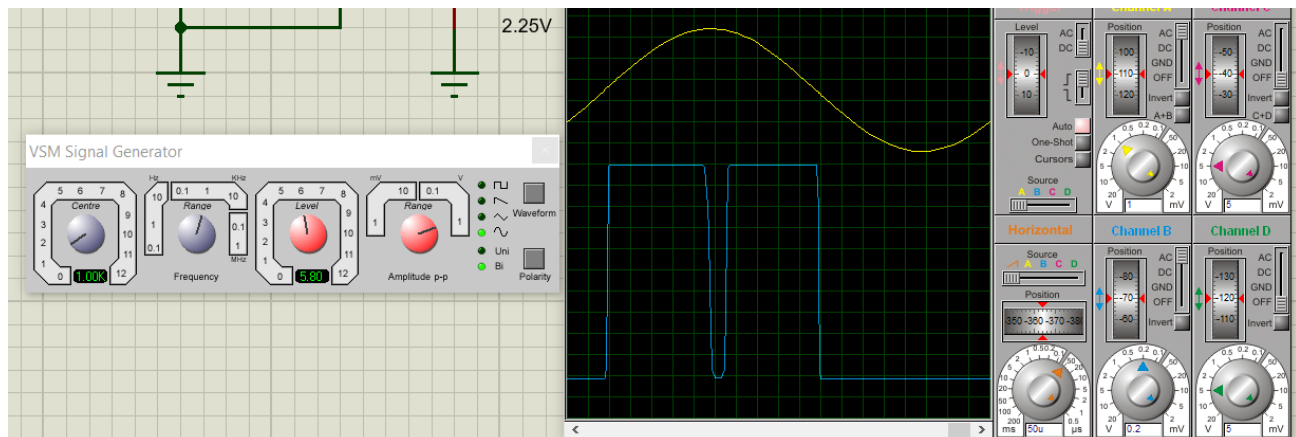- Start Distort, amplitude =  $\frac{5.80}{2} = 2.90$



Hence, the maximum amplitude of  $V_{in}$  before the  $V_o$  starts to distort is  $A = 2.85$ .